




Advancing EVSE Through Controller Hardware-in-the-Loop Validation

Sertac Bayhan, Ph.D.

AGENDA

- i. Introduction
- ii. C-HIL Setup
- iii. Considered Systems
- iv. Test Results
- v. Conclusion


INTRODUCTION – GENERAL STRUCTURE

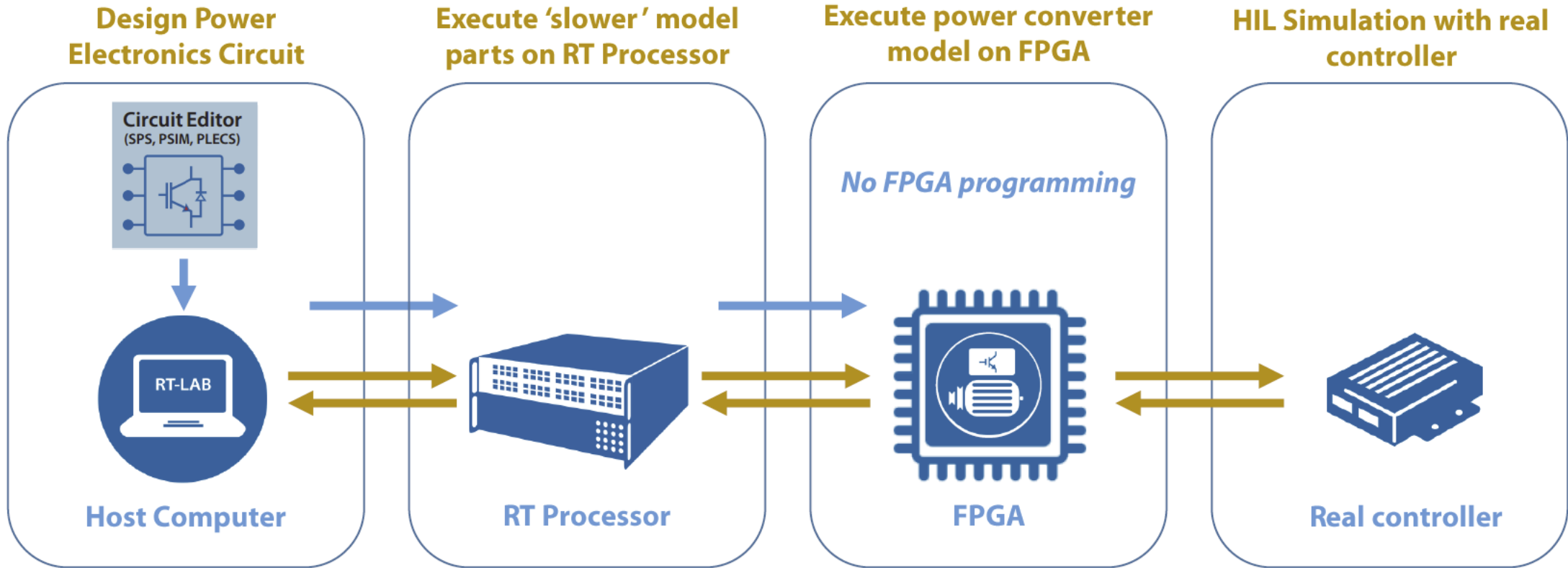




FPGA model:

- Fast electrical circuit (user model)
- Runs in the FPGA (typical $T_s < 1 \mu S$)
- Is connected with the CPU model
- Is connected with hardware I/Os

STRUCTURE – INTERNAL STRUCTURE

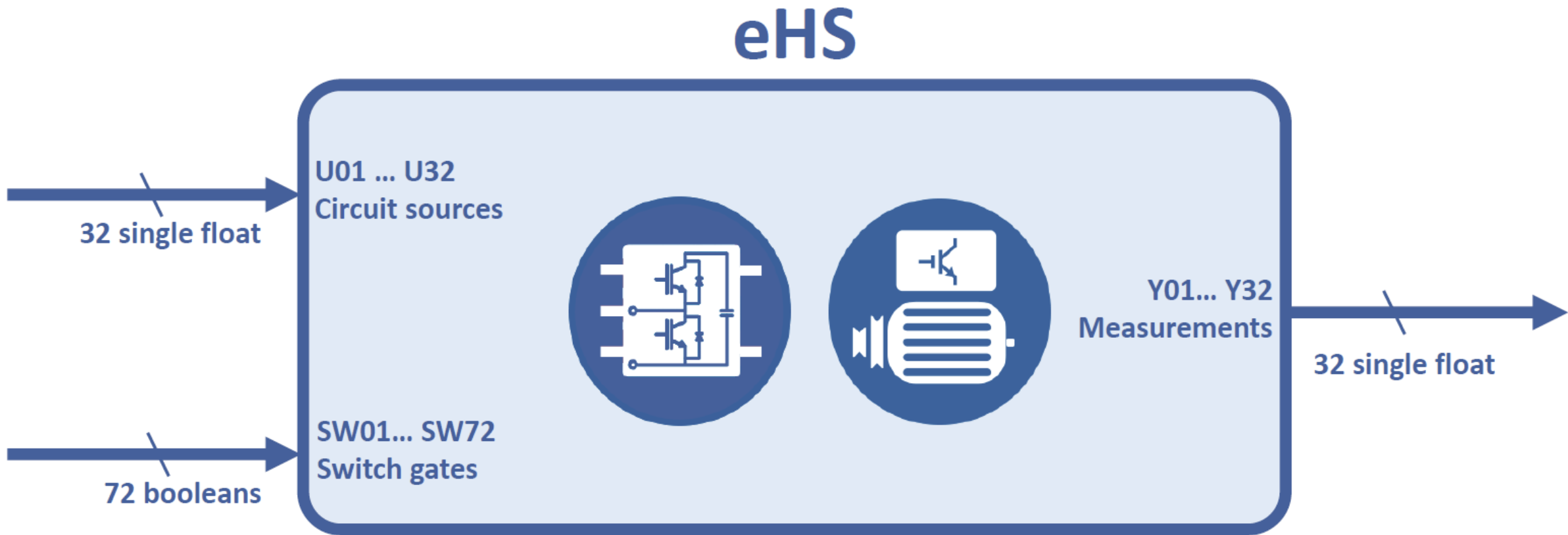


CHIL and PHIL Setup at QEERI

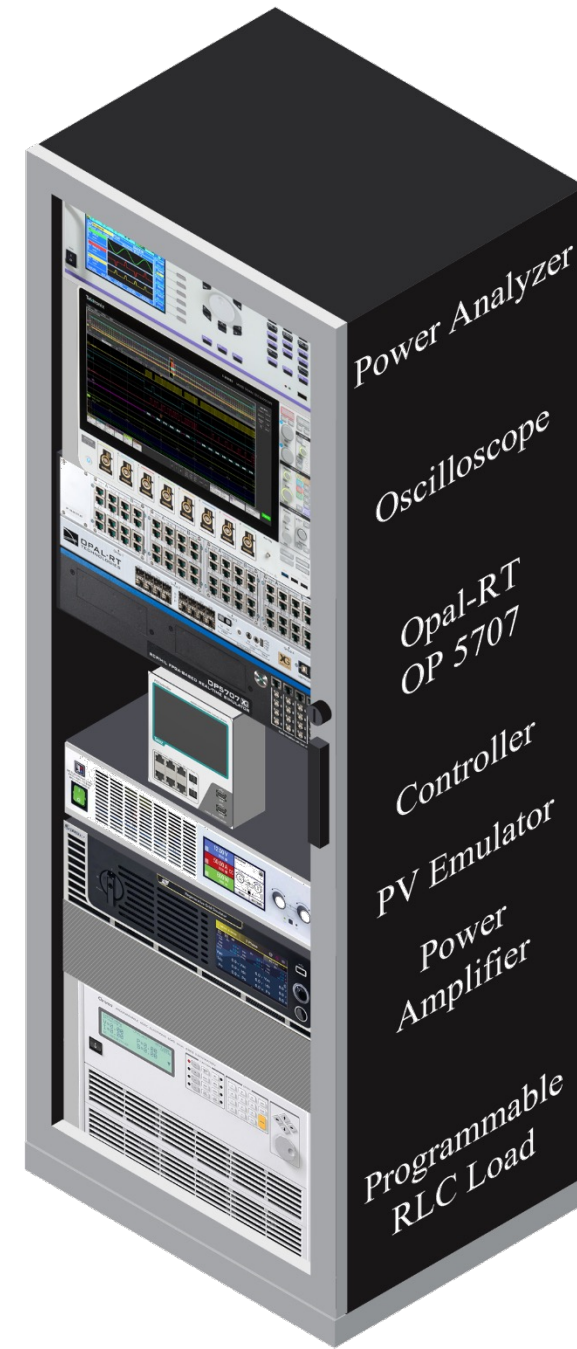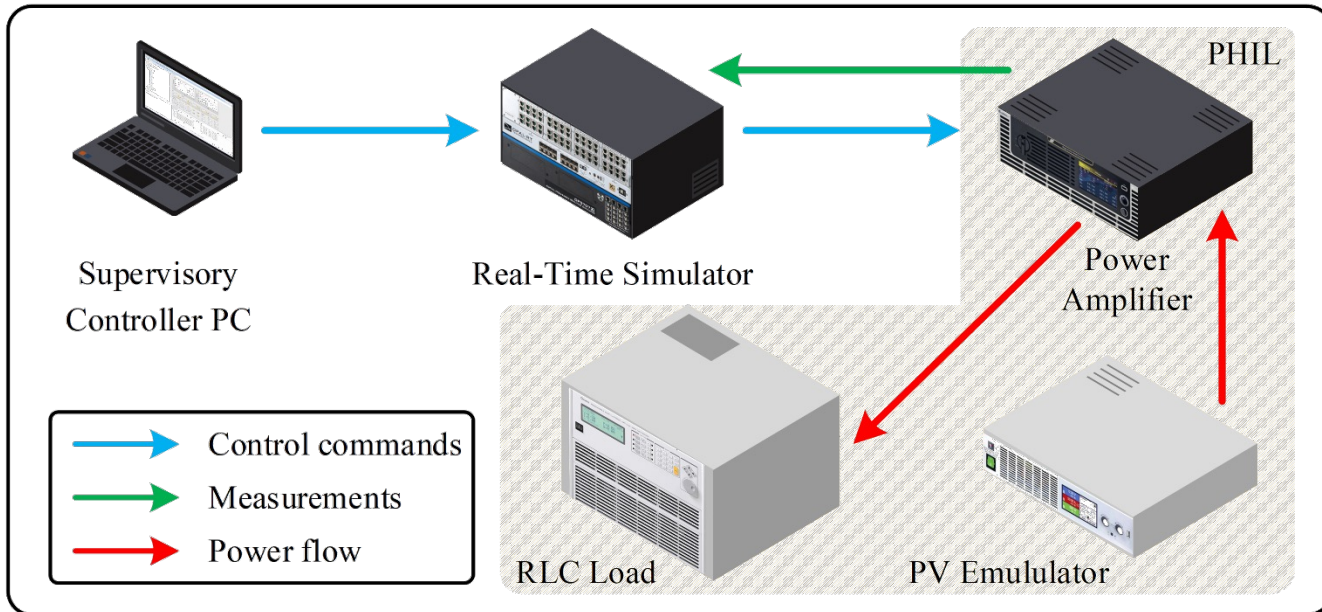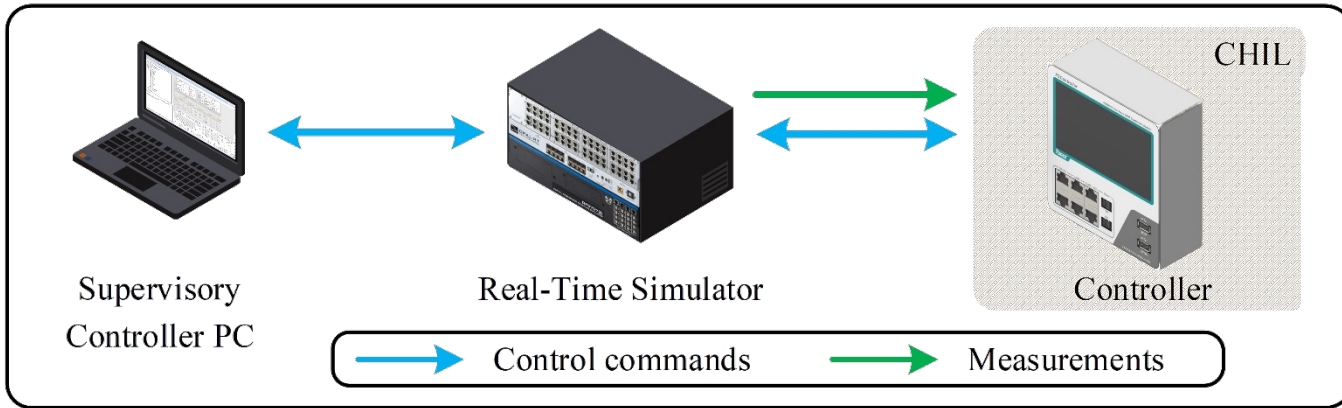

Controller Specs


01. 5" Touch Display for GUI & Control

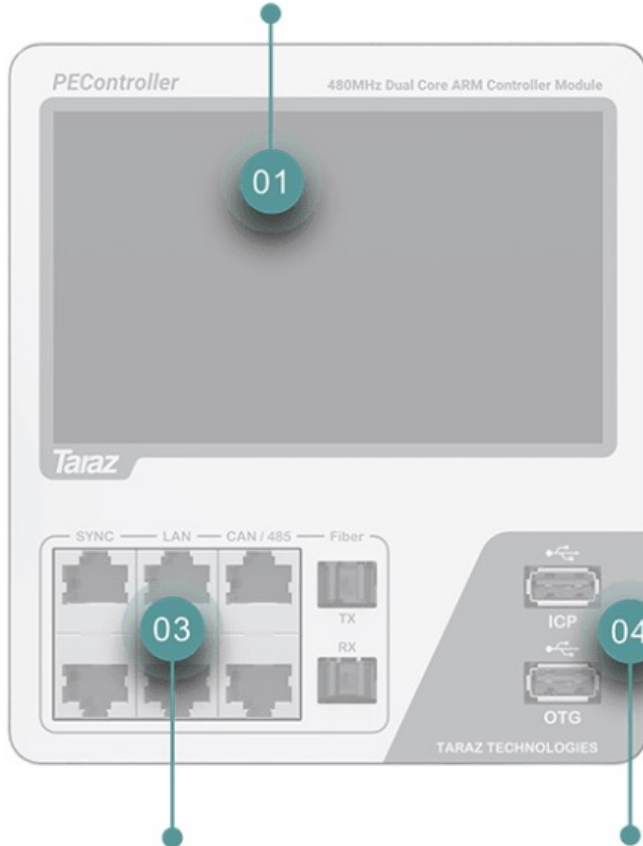

03. Sync, LAN, CAN, RS-485 & Fiber Optics for Industrial Communication & Distributed Control System

04. Programming USB & High-Speed USB for Data Acquisition

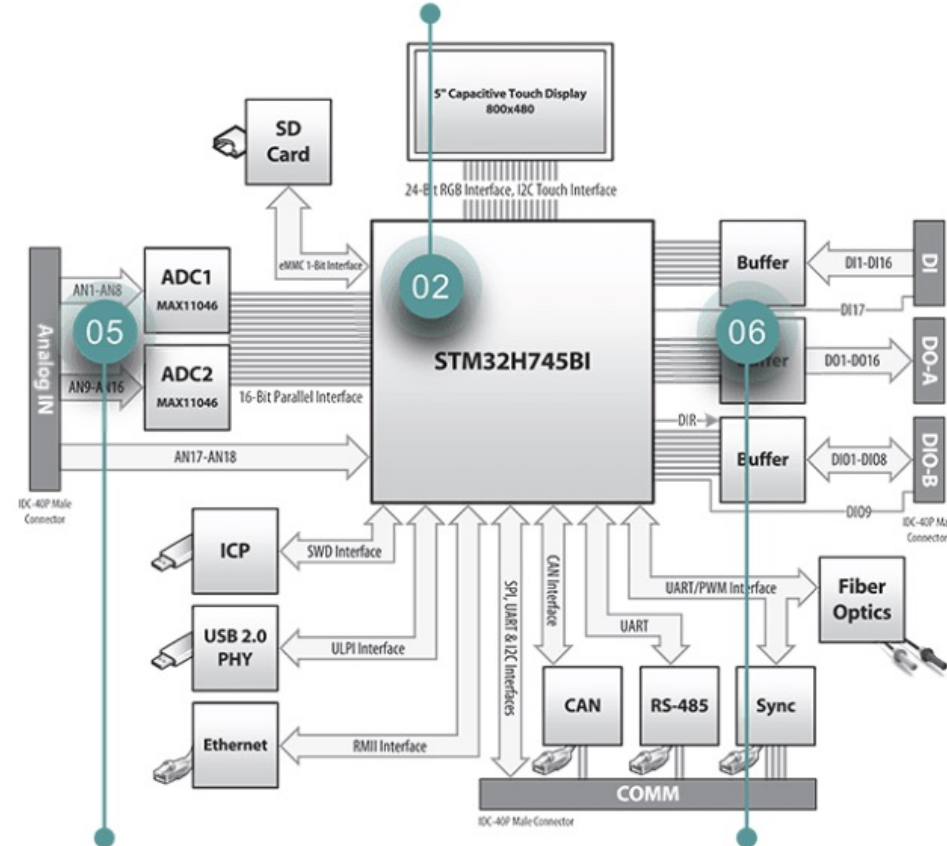02. High-Performance Dual-Core 480MHz (M7) /240MHz (M4) Microcontroller



05. High Accuracy 16CH @ 16-Bit, Simultaneous Sampling ADCs for High-Performance Control

06. Upto 68 I/Os Including 24 PWMs, 18 Analog Inputs, Quadrature Encoder, SPI, UART & I2C Interfaces

FRONT PANEL

ARCHITECTURE

Considered System

DC EVSE


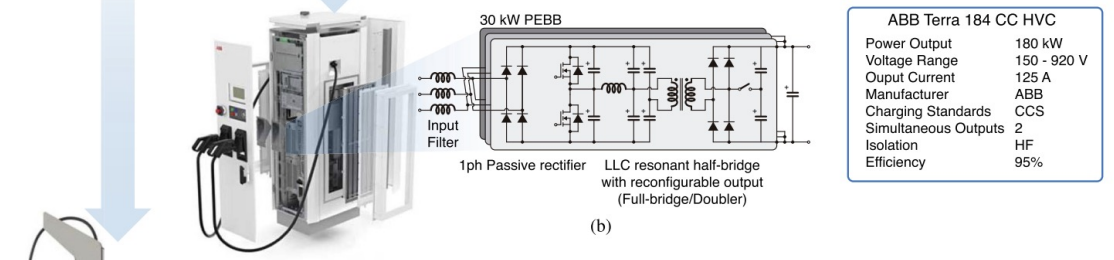
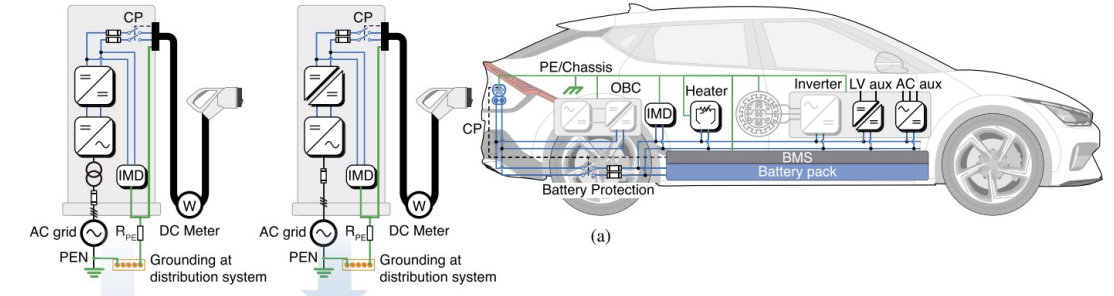
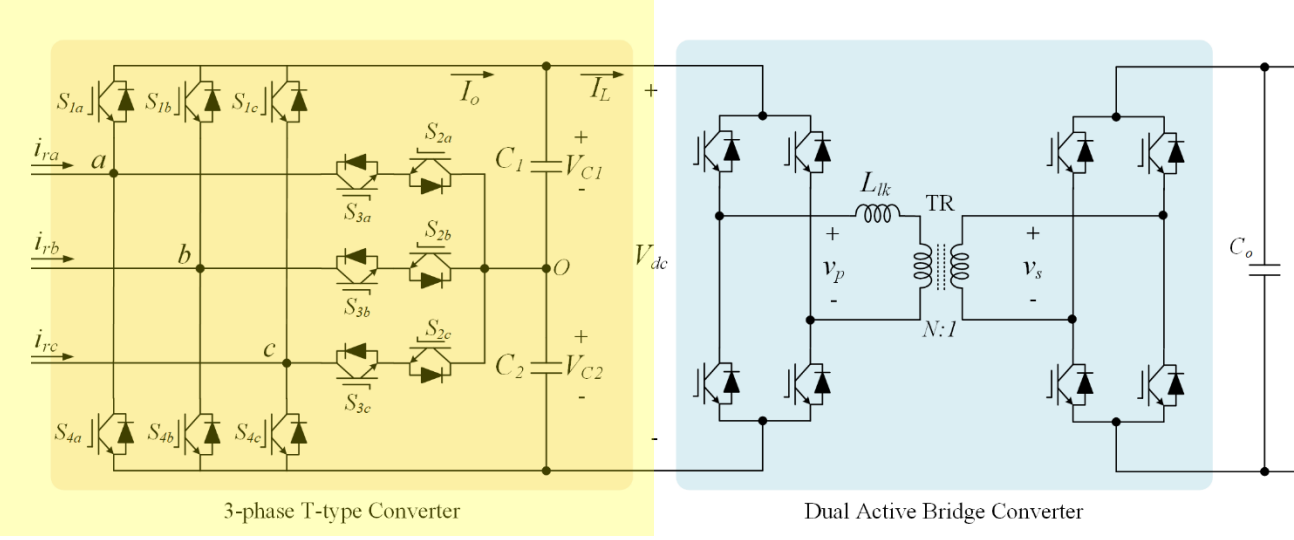
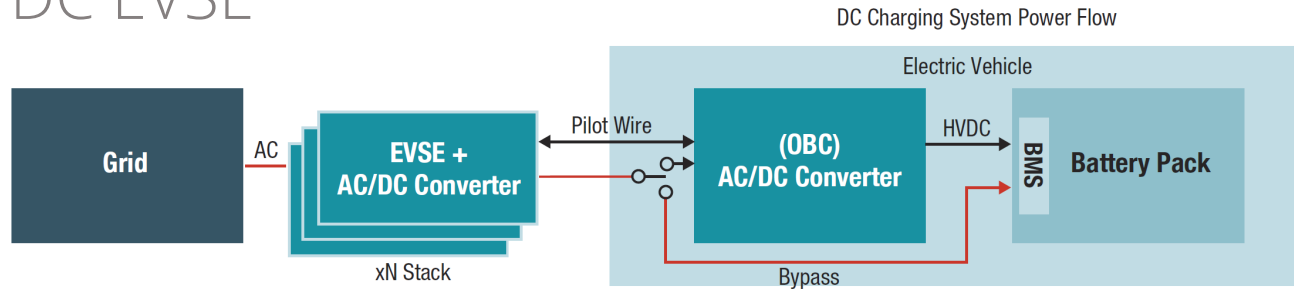



ABB Terra 184 CC HVC	
Power Output	180 kW
Voltage Range	150 - 920 V
Output Current	125 A
Manufacturer	ABB
Charging Standards	CCS
Simultaneous Outputs	2
Isolation	HF
Efficiency	95%

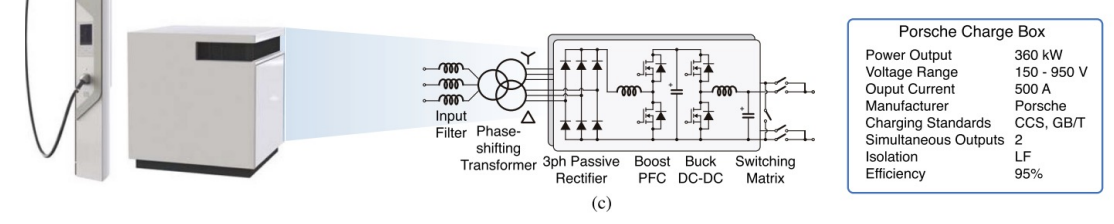


Porsche Charge Box	
Power Output	360 kW
Voltage Range	150 - 950 V
Output Current	500 A
Manufacturer	Porsche
Charging Standards	CCS, GB/T
Simultaneous Outputs	2
Isolation	LF
Efficiency	95%

S. Rivera *et al.*, "Charging Infrastructure and Grid Integration for Electromobility," in *Proceedings of the IEEE*, vol. 111, no. 4, pp. 371-396, April 2023, doi: 10.1109/JPROC.2022.3216362.

Control Technique

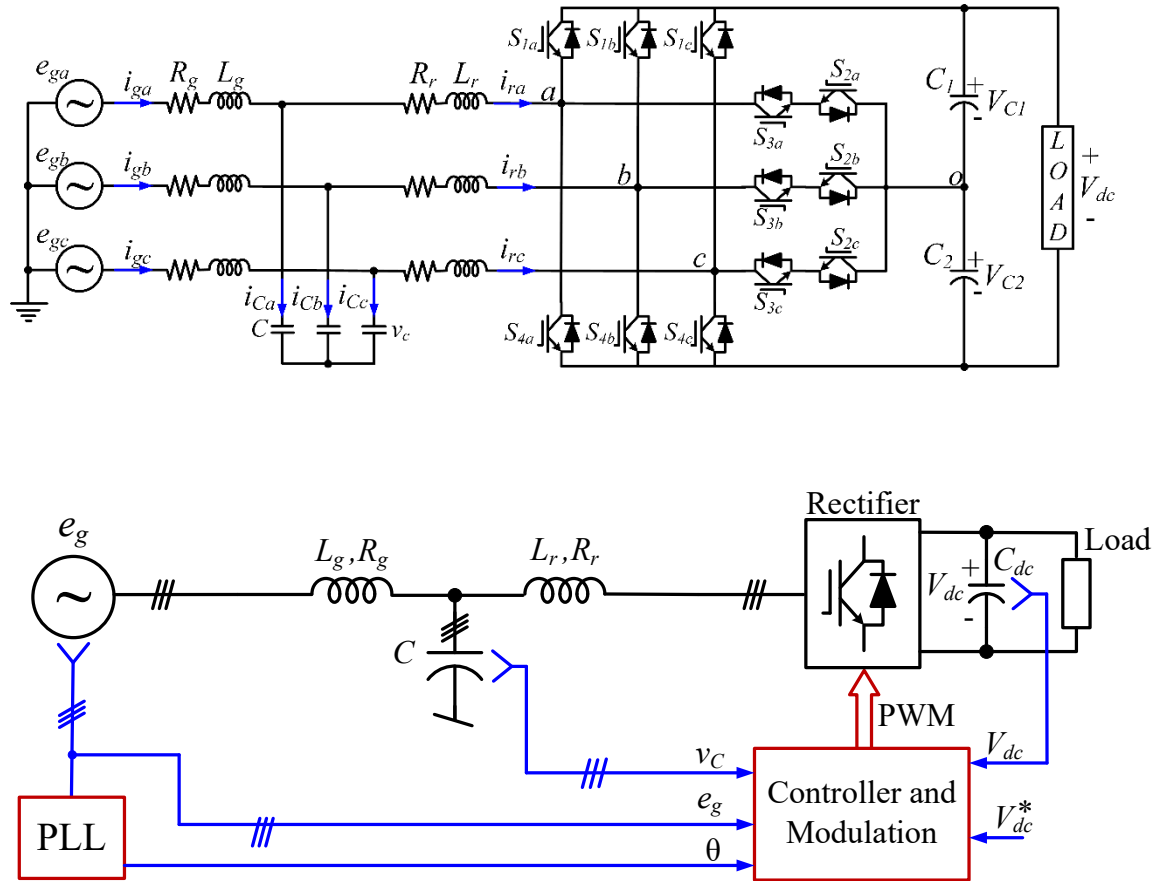


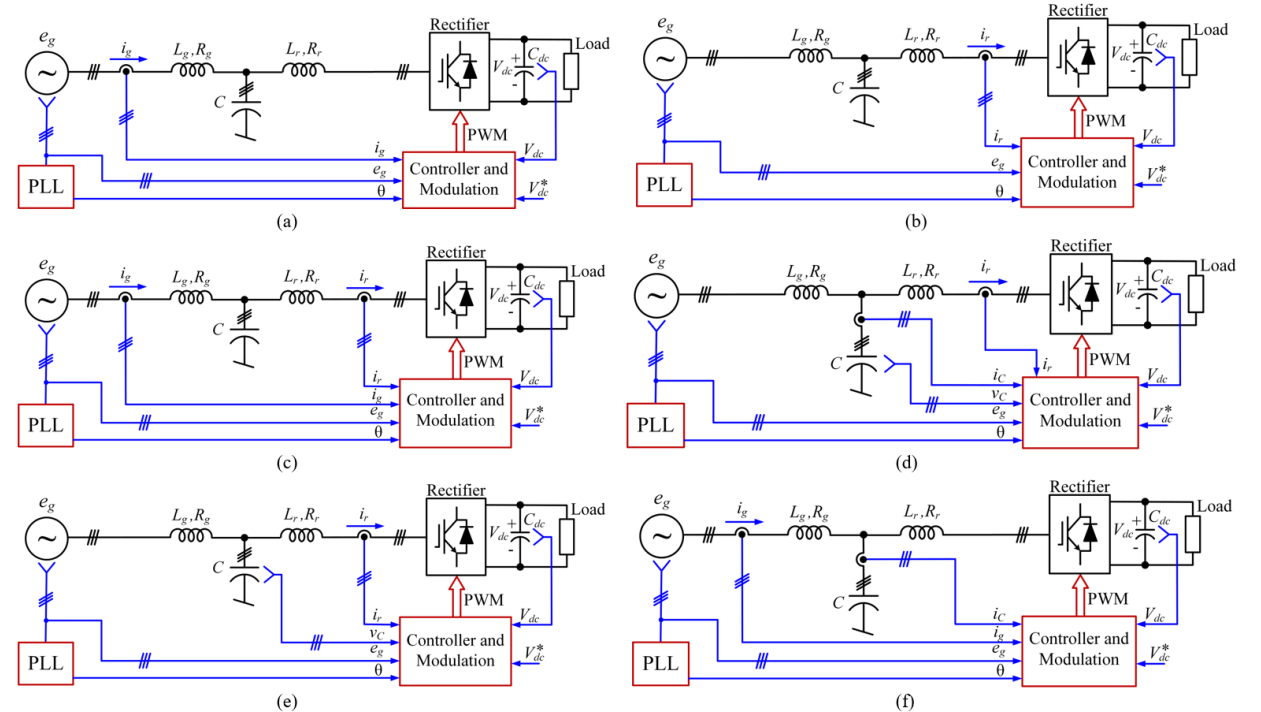Block diagram of the proposed current sensorless control technique



Block diagrams of existing control methods for three-phase active front-end rectifier with LCL filter. (a) grid current feedback, (b) rectifier current feedback, (c) grid current and rectifier current feedbacks, (d) rectifier current, capacitor current and capacitor voltage feedbacks, (e) rectifier current and capacitor voltage feedbacks and (f) grid current and capacitor current feedbacks.


Control Technique

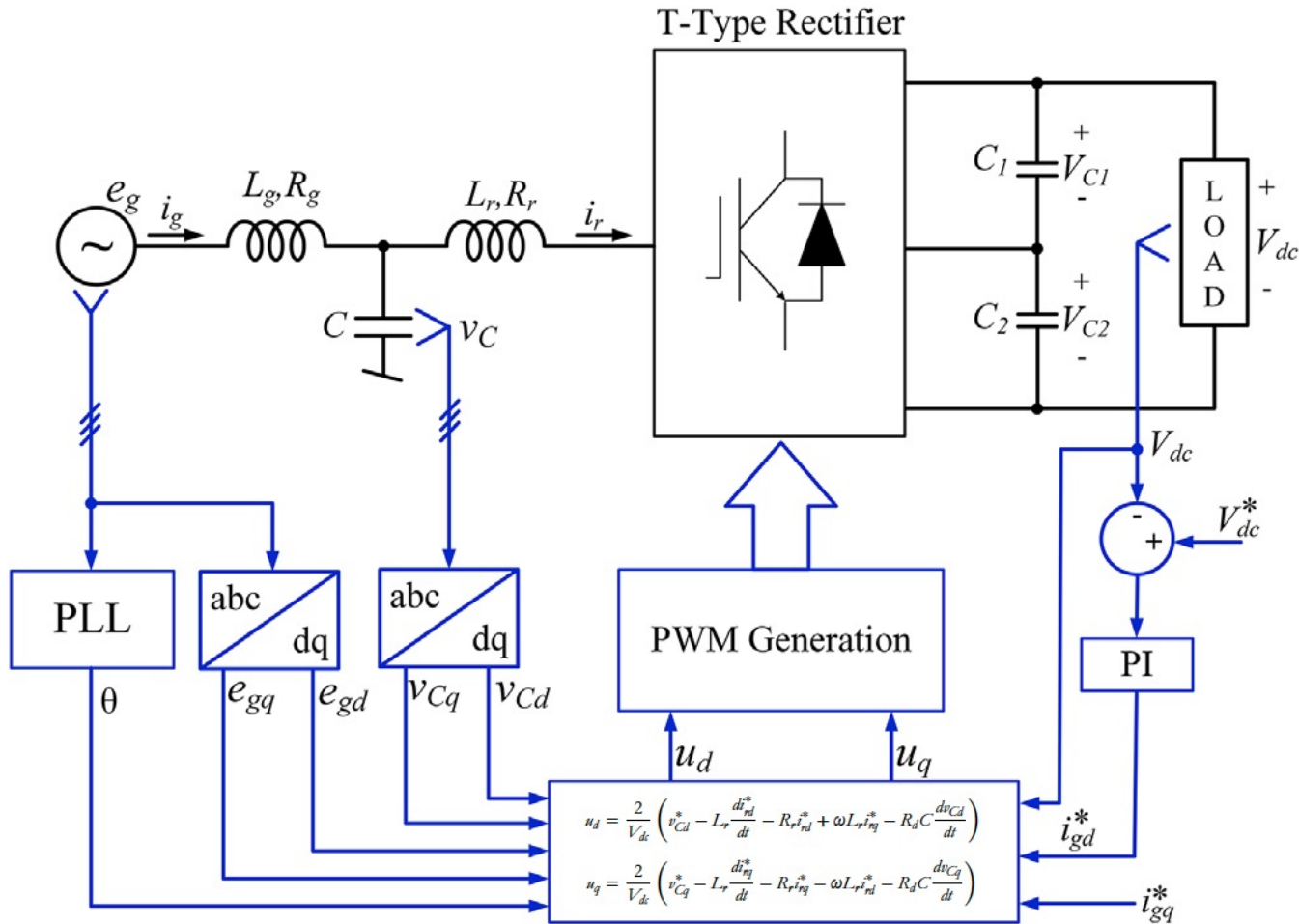


SYSTEM AND CONTROL PARAMETERS

Description and Symbol	Value
Grid voltage amplitude, E_m	$120\sqrt{2}$ V
DC-link voltage reference, V_{dc}^*	400V
Grid-side inductance, L_g	2.5mH
Rectifier-side inductance, L_r	5mH
Inductor resistances, R_g and R_r	0.4Ω, 0.5Ω
Filter capacitor, C	22μF
DC capacitors, $C_1 = C_2$	470μF
Load	40 Ω - 80 Ω
Virtual damping resistor, R_d	8Ω
PI gains, K_p and K_i	0.04, 10
Sampling period: T_s	40μs


Test Results

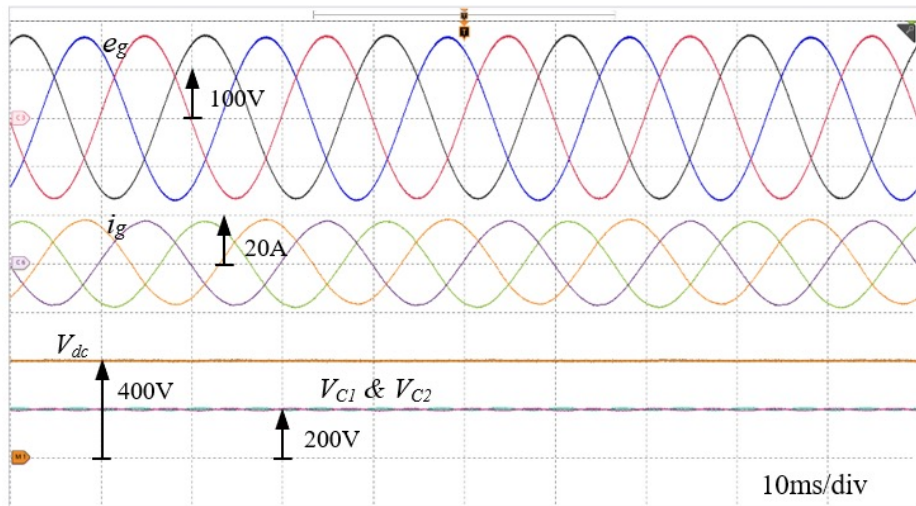

(a)

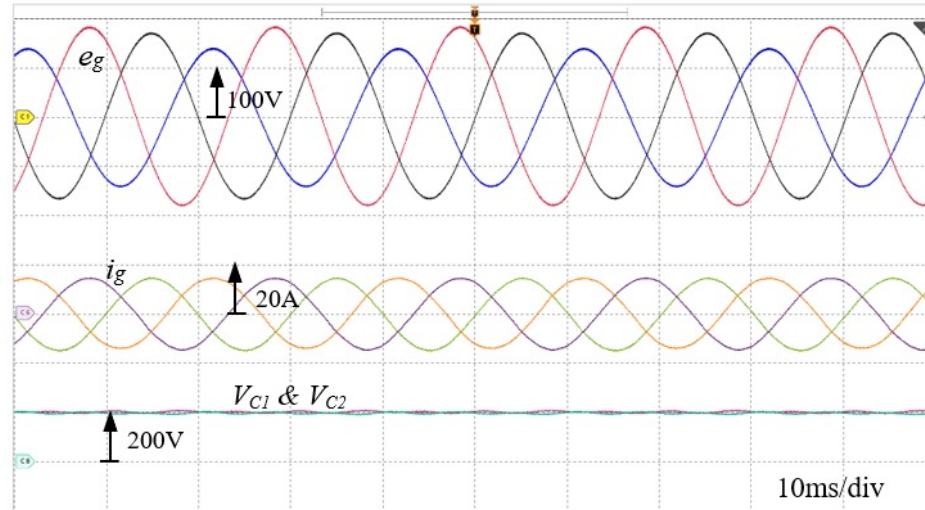


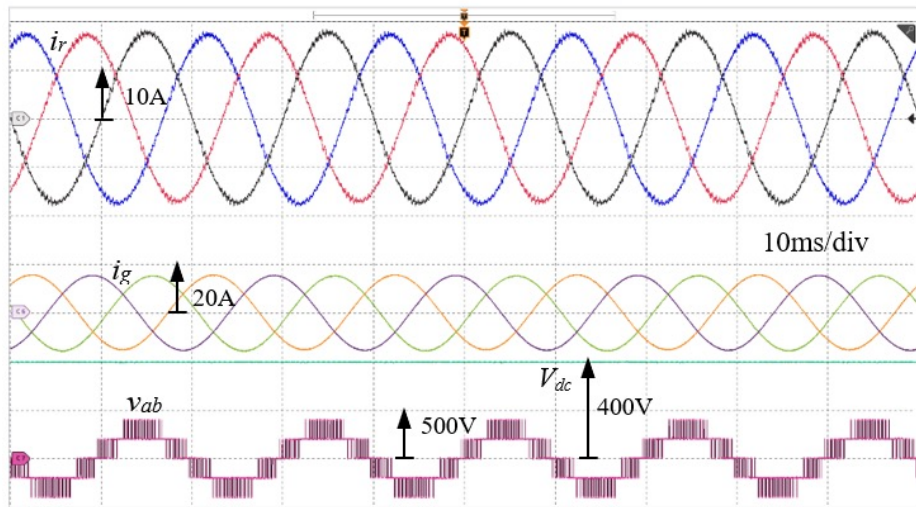Steady-state responses of dc- and ac-side variables under unbalanced grid.




(b)

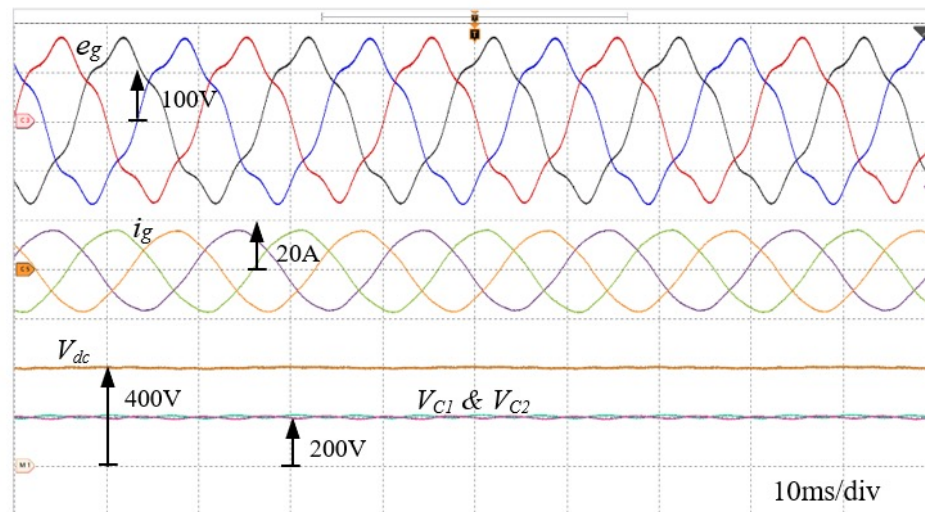Steady-state responses of dc- and ac-side variables under balanced grid.




Steady-state responses of dc- and ac-side variables under distorted grid.



Test Results

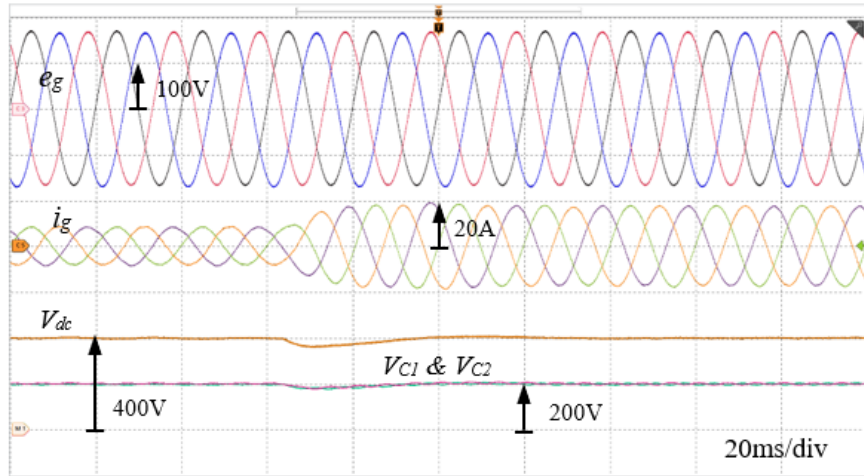

(a)

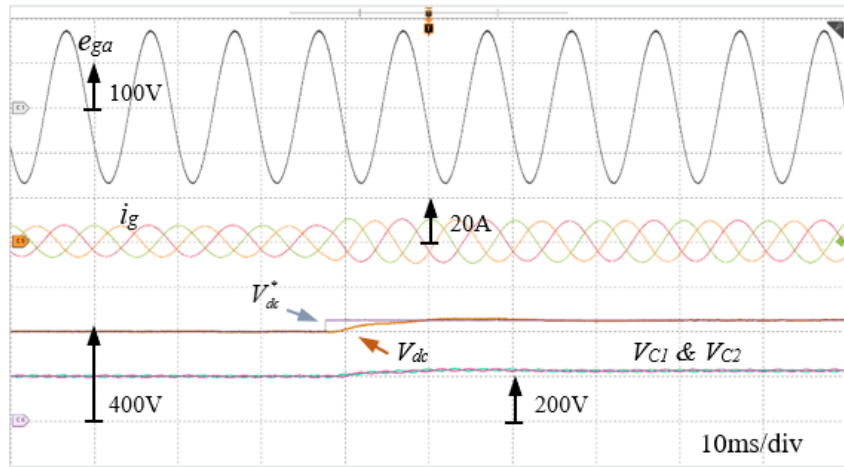


(b)

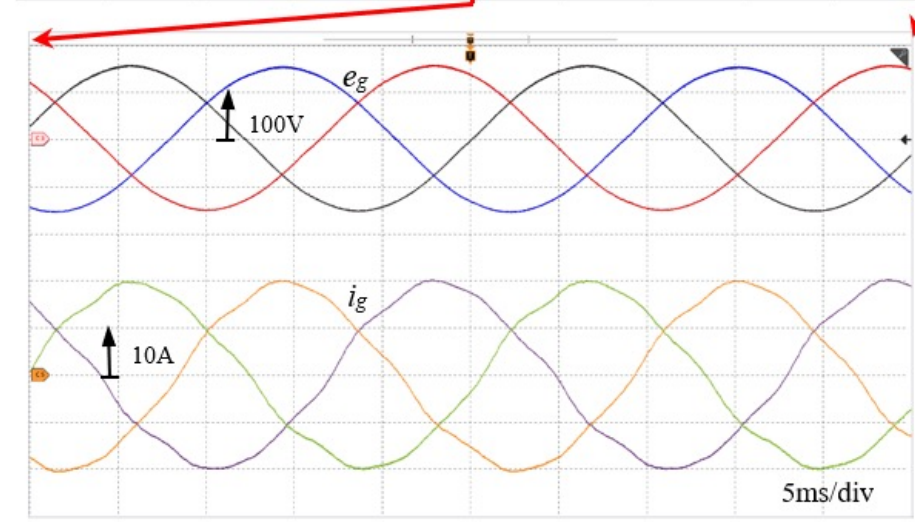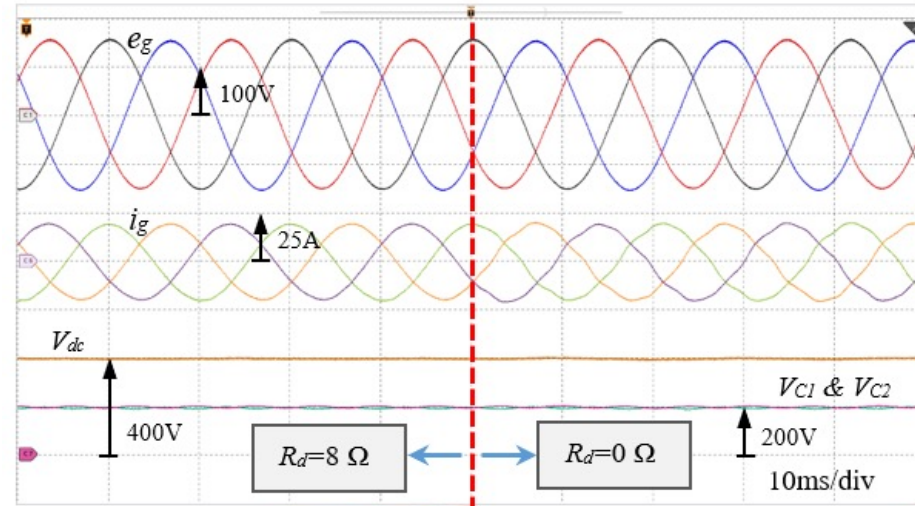


Responses of dc-and ac-side variables for a step change in R_d from $8\ \Omega$ to $0\ \Omega$.

Dynamic responses of dc-and ac-side variables for a step change in load resistance from $80\ \Omega$ to $40\ \Omega$ and V_{dc}^* from 400V to 450V.



Test Results

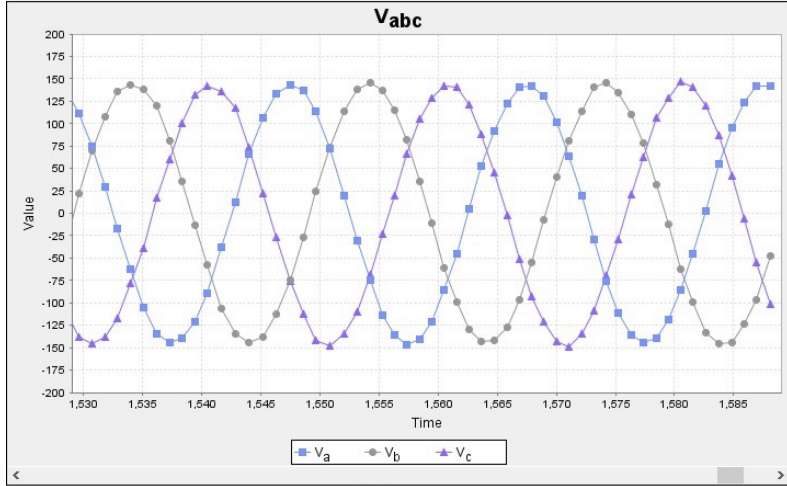


(1)

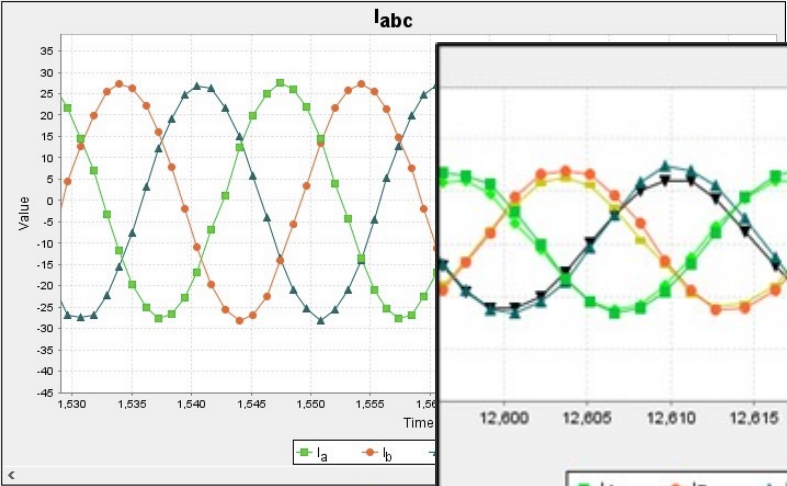

(2)

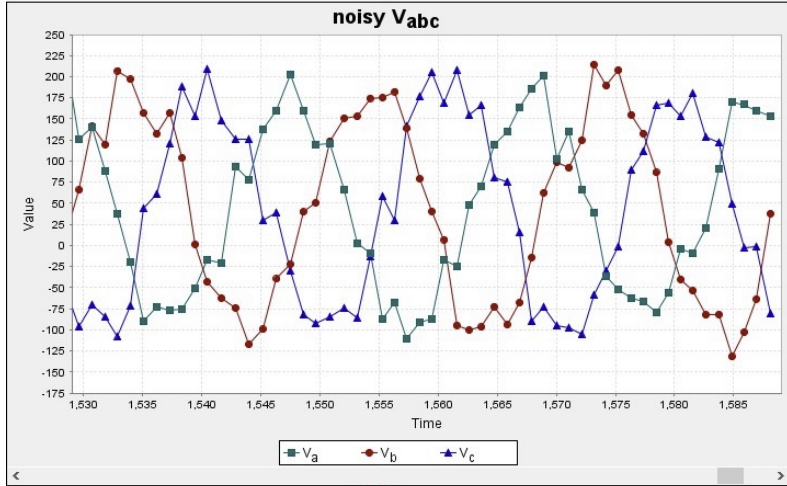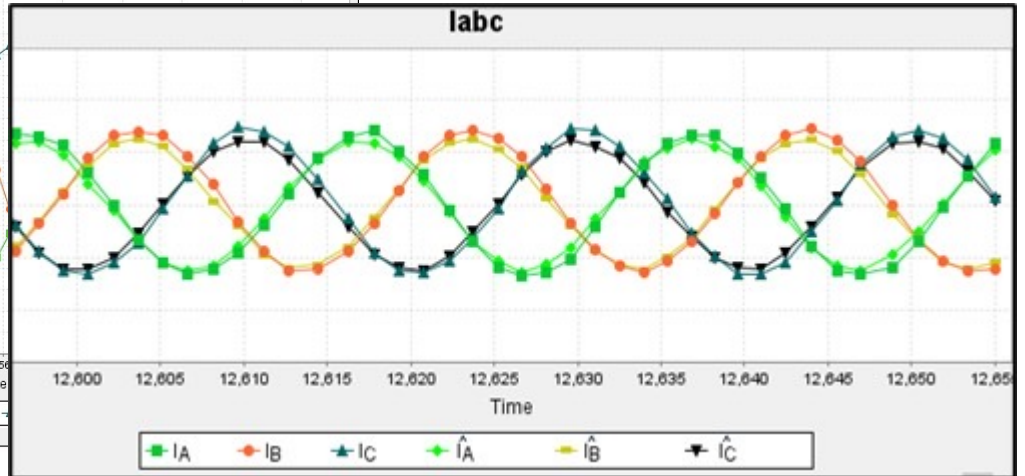


(3)

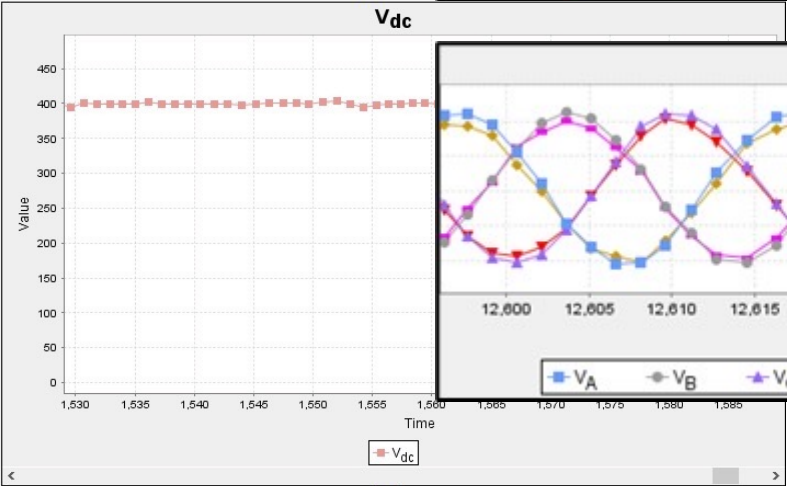


(4)


Control Technique

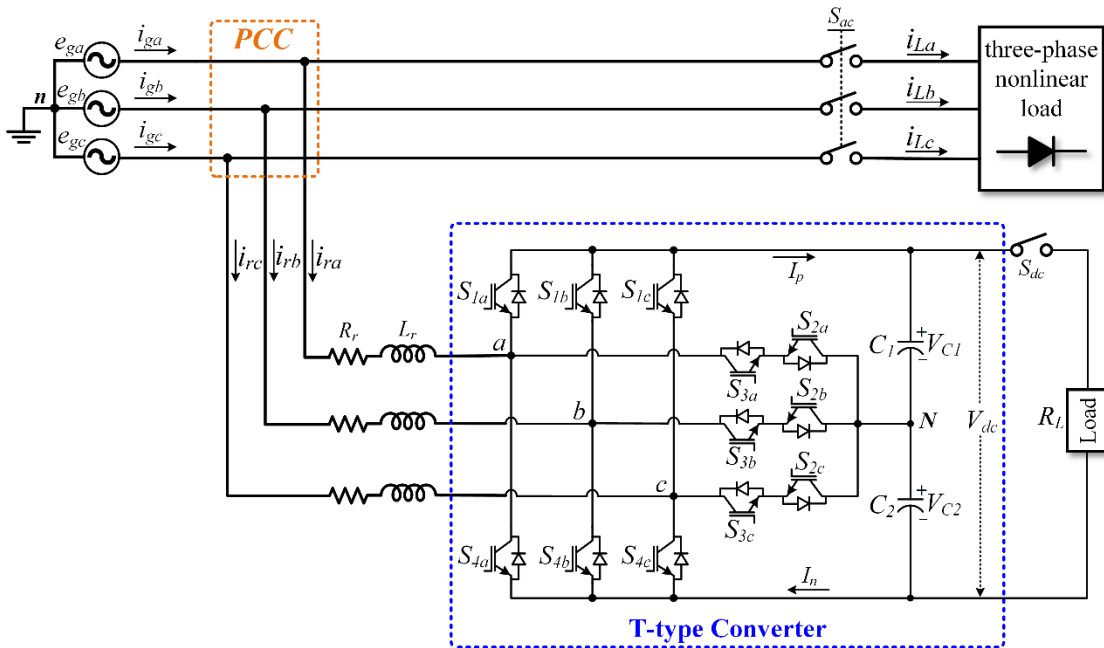

OPAL-RT

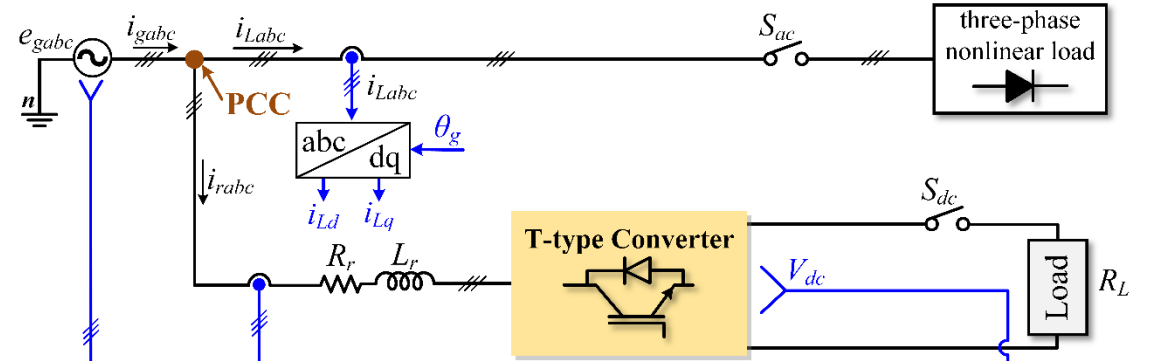

PEController

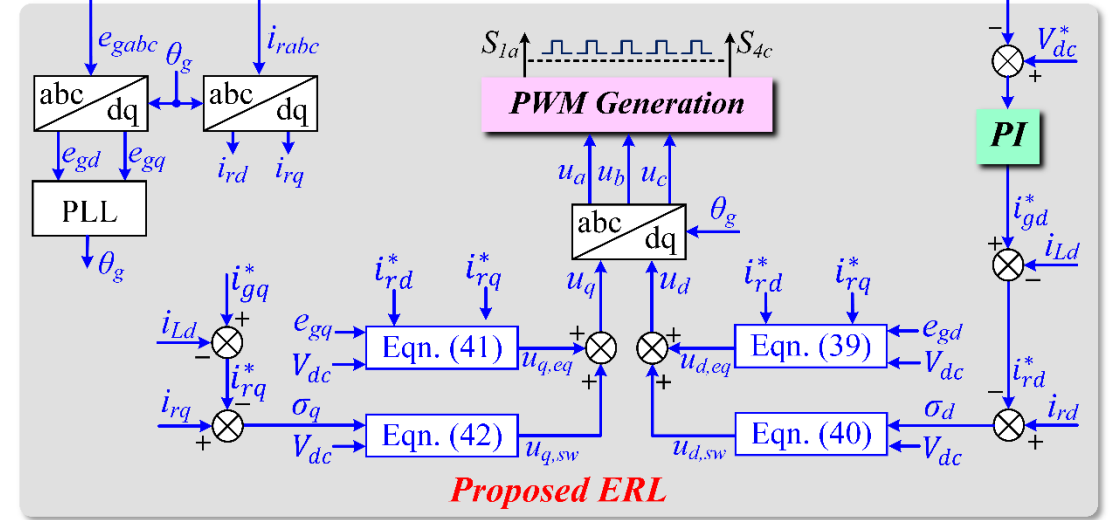


$$u_{q,eq} = \frac{2}{V_{dc}} \left(e_{gq} - L_r \frac{di_{rq}^*}{dt} - R_r i_{rq}^* - \omega L_r i_{rd}^* \right)$$

$$u_{d,eq} = \frac{2}{V_{dc}} \left(e_{gd} - L_r \frac{di_{rd}^*}{dt} - R_r i_{rd}^* + \omega L_r i_{rq}^* \right)$$


$$u_{q,sw} = \frac{2L_r k_1}{V_{dc}} \left(k_2 e^{k_3 \sigma_q} - 1 \right)$$

$$u_{d,sw} = \frac{2L_r k_1}{V_{dc}} \left(k_2 e^{k_3 \sigma_d} - 1 \right)$$

Test Results

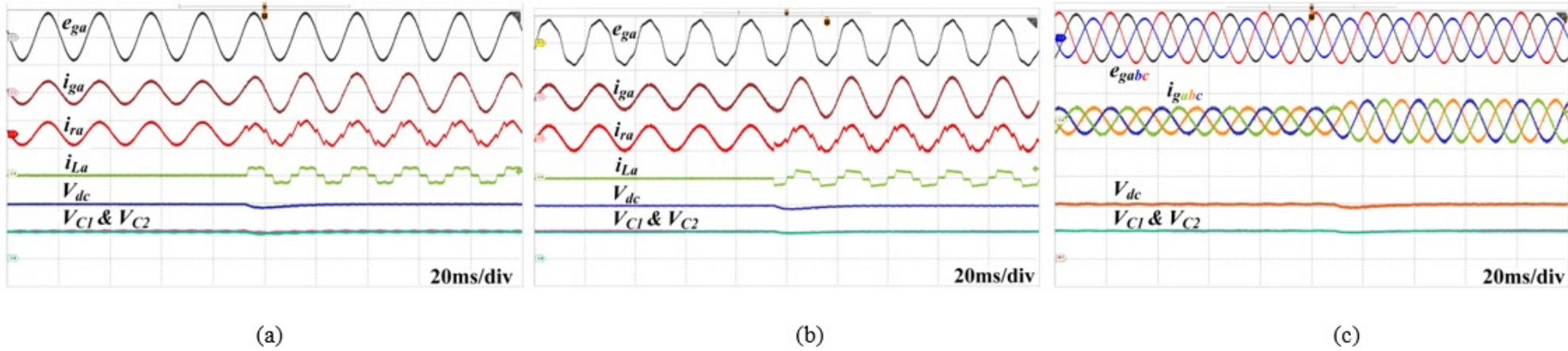


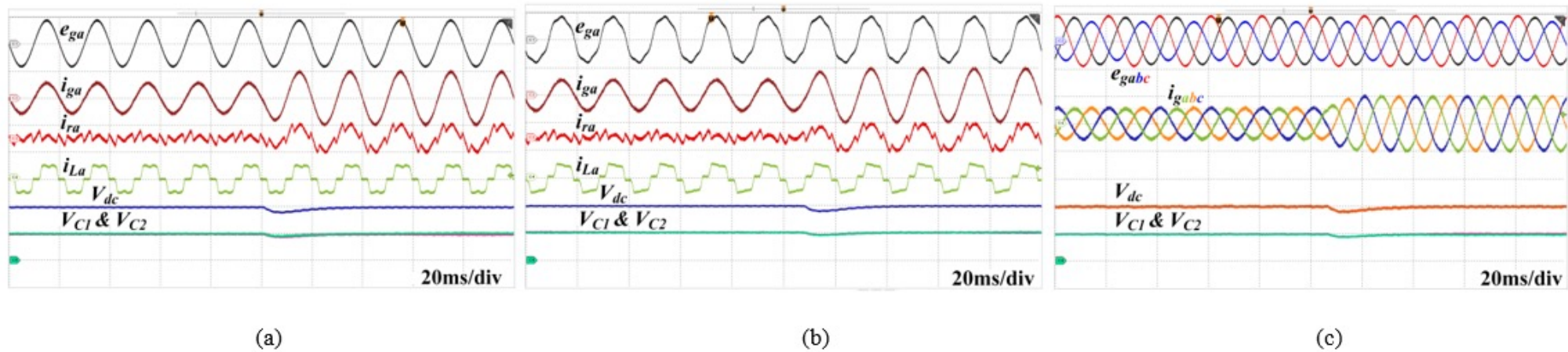Waveforms for scenario 1. (a) Non-distorted and balanced grid, (b) Distorted and balanced grid, (c) Non-distorted and unbalanced grid. e_{ga}, e_{gabc} (200V/div), $i_{ga}, i_{gabc}, i_{ra}, i_{La}$ (20A/div), and V_{dc}, V_{C1}, V_{C2} (250V/div).



Waveforms for scenario 2. (a) Non-distorted and balanced grid, (b) Distorted and balanced grid, (c) Non-distorted and unbalanced grid. e_{ga}, e_{gabc} (200V/div), $i_{ga}, i_{gabc}, i_{ra}, i_{La}$ (20A/div), and V_{dc}, V_{C1}, V_{C2} (250V/div).

Test Results

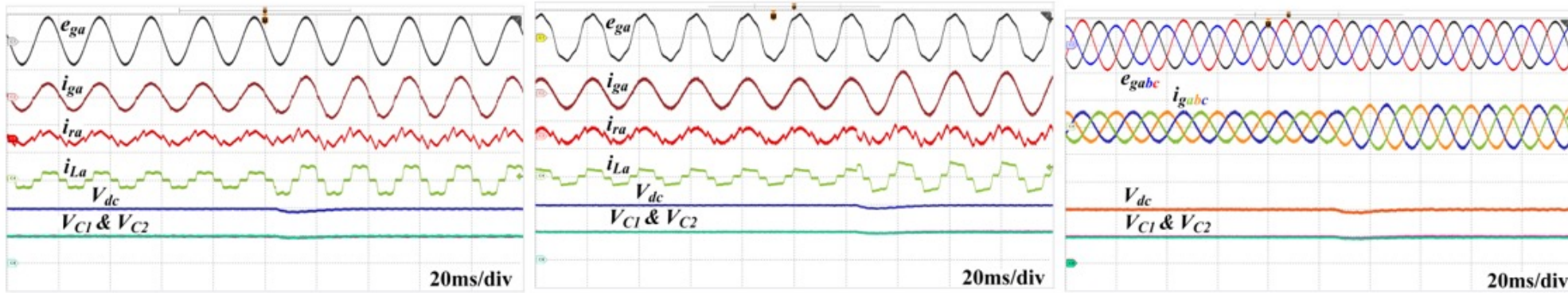


(a)

(b)

(c)

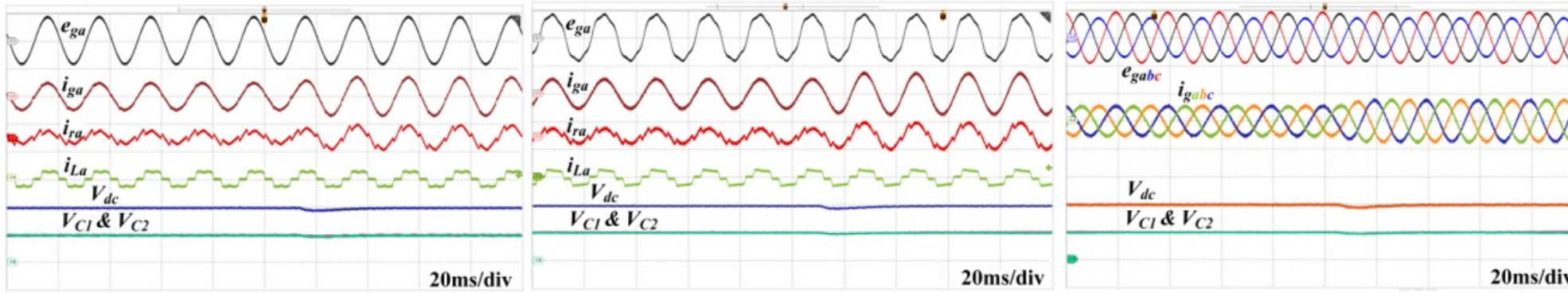Waveforms for scenario 3. (a) Non-distorted and balanced grid, (b) Distorted and balanced grid, (c) Non-distorted and unbalanced grid. e_{ga}, e_{gabc} (200V/div), $i_{ga}, i_{gabc}, i_{ra}, i_{La}$ (20A/div), and V_{dc}, V_{C1}, V_{C2} (250V/div).



(a)

(b)

(c)


Waveforms for scenario 4. (a) Non-distorted and balanced grid, (b) Distorted and balanced grid, (c) Non-distorted and unbalanced grid. e_{ga}, e_{gabc} (200V/div), $i_{ga}, i_{gabc}, i_{ra}, i_{La}$ (20A/div), and V_{dc}, V_{C1}, V_{C2} (250V/div).

Conclusion

- ❑ C-HIL validation is a transformative approach that holds immense promise in advancing the development of power electronic converters for EVSE.
- ❑ C-HIL validation accelerates development processes by facilitating rapid prototyping and optimization of control algorithms, resulting in more efficient and reliable converter designs.
- ❑ It contributes to the creation of robust and resilient converter designs by evaluating controller responses to fault conditions, ensuring adaptability to unforeseen challenges.
- ❑ The validation method supports bidirectional power flow control, paving the way for advanced functionalities like vehicle-to-grid (V2G) services and efficient energy management.
- ❑ By bridging the gap between theoretical models and physical prototypes through hardware integration, C-HIL validation enhances the accuracy of converter testing and validation.

essentially,
all models are wrong,
but some are useful

George E. P. Box

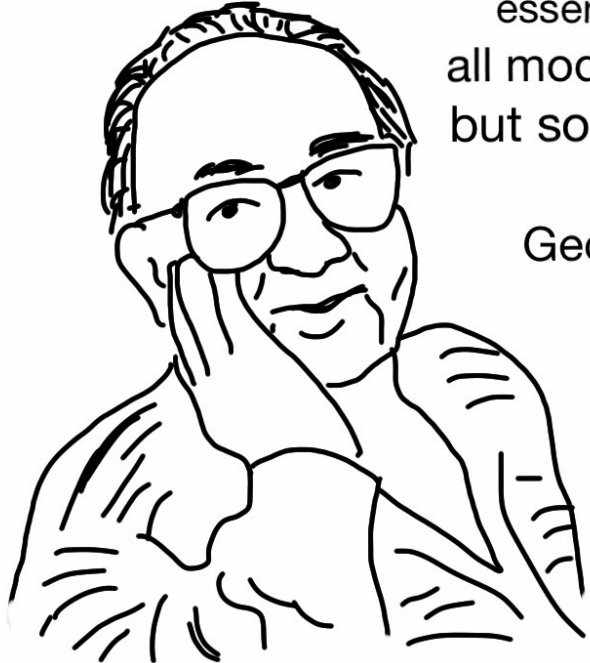

Q&A